

# VU Quiz Collection

Generated by Firewall Bypass VU Extension

## VU Quiz Collection

Total Quizzes: 10

Courses: CS302 - Digital Logic Design (Semester Quiz # 02), CS301

Generated: 26/11/2025, 22:24:18

Powered by Firewall Bypass VU Extension

Waseem Akram | wasii.dev | +1 (204) 813-2846

## Quiz 1 - CS302 - Digital Logic Design (Semester Quiz # 02)

### Question:

In a 4-variable K-map, a 2-variable product term is produced by

### Options:

- A. a 8-cell group of 1s
- B. a 2-cell group of 1s
- C. a 4-cell group of 1s
- D. a 4-cell group of 0s

Copied: 25/11/2025, 10:55:35

## Quiz 2 - CS302 - Digital Logic Design (Semester Quiz # 02)

### Question:

The look-ahead carry circuits\_\_\_\_\_

### Options:

- A. Add a 1 to complemented inputs
- B. Increase ripple delay
- C. Determine sign and magnitude
- D. Reduce propagation delay

Copied: 25/11/2025, 10:55:53

## Quiz 3 - CS302 - Digital Logic Design (Semester Quiz # 02)

### Question:

The boolean expression  $A + BC$  equals

### Options:

- A.  $(A' + B)(A' + C)$

B.  $(A + B')(A + C')$

C.  $(A + B)(A + C)$

D.  $(A + B)(A' + C)$

Copied: 25/11/2025, 10:56:05

## Quiz 4 - CS302 - Digital Logic Design (Semester Quiz # 02)

### Question:

The Adjacent 1s Detector accepts 4-bit inputs. If \_\_\_\_\_ adjacent 1s are detected in the input, the output is set to high.

### Options:

A. 2

B. 1

C. 4

D. 0

Copied: 25/11/2025, 10:56:18

## Quiz 5 - CS302 - Digital Logic Design (Semester Quiz # 02)

### Question:

\_\_\_\_\_ single digit BCD Adders can be cascaded together to form a 2-digit BCD Adder.

### Options:

A. Two

B. Four

C. Three

D. One

Copied: 25/11/2025, 10:56:26

## Quiz 6 - CS302 - Digital Logic Design (Semester Quiz # 02)

### Question:

The \_\_\_\_\_ select input(s) of the two 4-input multiplexers are common in Dual 4-input multiplexer.

### Options:

- A. Three
- B. Two
- C. Four
- D. One

Copied: 25/11/2025, 10:56:34

## Quiz 7 - CS301

### Question:

If there is a complete binary tree of depth 4, the total number of nodes in it will be:

### Options:

- A. 31
- B. 33
- C. 32
- D. 30

Copied: 26/11/2025, 22:19:32

## Quiz 8 - CS301

### Question:

Binary search tree class is defined as a template class so that it can be used for \_\_\_\_\_ datatype(s).

### Options:

- A. Integer

B. Strings

C. Character

D. Any

Copied: 26/11/2025, 22:19:48

## Quiz 9 - CS301

### Question:

Which of the following condition will be true if a node is NULL during the in-order traversal using recursive calls?

### Options:

A. Node contains only left child

B. Node does not contain both left and right children

C. Node contains only right child

D. Node can contain only one child

Copied: 26/11/2025, 22:20:02

## Quiz 10 - CS301

### Question:

Which of the following is true about binary trees?

### Options:

A. Parent node of two sibling nodes must be same

B. A node can have multiple parent nodes

C. A binary tree should have only one leaf node

D. A binary tree should have two root nodes

Copied: 26/11/2025, 22:20:21